

SA's Leading Past Year

Exam Paper Portal



You have Downloaded, yet Another Great
Resource to assist you with your Studies 😊

Thank You for Supporting SA Exam Papers

Your Leading Past Year Exam Paper Resource Portal

Visit us @ www.saexampapers.co.za



**SA EXAM
PAPERS**



basic education

Department:
Basic Education
REPUBLIC OF SOUTH AFRICA

NATIONAL SENIOR CERTIFICATE

GRADE 12

ELECTRICAL TECHNOLOGY: ELECTRONICS

NOVEMBER 2019

MARKS: 200

TIME: 3 hours

**This question paper consists of 16 pages, a 1-page formula sheet and
6 answer sheets.**

INSTRUCTIONS AND INFORMATION

1. This question paper consists of FIVE questions.
2. Answer ALL the questions.
3. Answer the following questions on the attached ANSWER SHEETS:

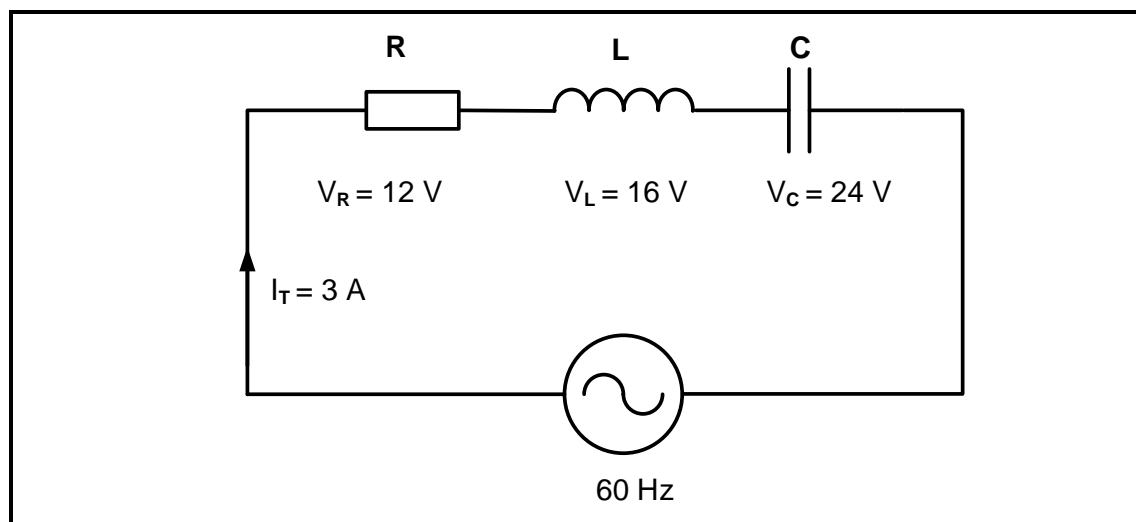
QUESTION 2.3.4
QUESTION 3.4.3
QUESTIONS 4.1.2, 4.4.2, 4.6.2 and 4.7.3
QUESTIONS 5.4.1, 5.4.2, 5.6.4, 5.6.5 and 5.11.4
4. Write your CENTRE NUMBER and EXAMINATION NUMBER on every ANSWER SHEET and hand them in with your ANSWER BOOK, whether you have used them or not.
5. Sketches and diagrams must be large, neat and FULLY LABELLED.
6. Show ALL calculations and round off answers correctly to TWO decimal places.
7. Number the answers correctly according to the numbering system used in this question paper.
8. You may use a non-programmable calculator.
9. Calculations must include:
 - 9.1 Formulae and manipulations where needed
 - 9.2 Correct replacement of values
 - 9.3 Correct answer and relevant units where applicable
10. A formula sheet is attached at the end of this question paper.
11. Write neatly and legibly.

QUESTION 1: OCCUPATIONAL HEALTH AND SAFETY

- 1.1 Describe how *teamwork* improves work ethics. (2)
- 1.2 With reference to the Occupational Health and Safety Act, 1993 (Act 85 of 1993):
- 1.2.1 State TWO purposes of the Occupational Health and Safety Act, 1993 (Act 85 of 1993). (2)
- 1.2.2 Define the term *workplace*. (2)
- 1.3 An employer has a duty to report on occupational health and safety and related matters. Name ONE person they should inform when:
- 1.3.1 The allocated task is hazardous (1)
- 1.3.2 A major incident occurs (1)
- 1.4 State TWO general emergency procedures to be followed when the emergency siren is sounded at school. (2)
- [10]**

QUESTION 2: RLC CIRCUITS

- 2.1 Define the following with reference to RLC circuits:
- 2.1.1 Power factor (2)
- 2.1.2 Q-factor of an inductor in a resonant circuit (2)
- 2.2 State TWO applications of RLC circuits. (2)
- 2.3 FIGURE 2.3 below shows an RLC series circuit. Answer the questions that follow.

**FIGURE 2.3: RLC SERIES CIRCUIT**

Given:

$$\begin{aligned} I_T &= 3 \text{ A} \\ V_R &= 12 \text{ V} \\ V_L &= 16 \text{ V} \\ V_C &= 24 \text{ V} \\ f &= 60 \text{ Hz} \end{aligned}$$

- 2.3.1 Calculate the total voltage of the supply. (3)
- 2.3.2 Calculate the value of the inductive reactance. (3)
- 2.3.3 State if the circuit is capacitive or inductive. Motivate your answer. (2)
- 2.3.4 Complete the phasor diagram on the ANSWER SHEET for QUESTION 2.3.4 and show the direction of rotation. (4)
- 2.3.5 Describe how an increase in impedance, while keeping the resistance constant, will affect the phase angle and the power factor. (2)

- 2.4 FIGURE 2.4 below shows an RLC parallel circuit consisting of a $20\ \Omega$ resistor, an inductor with an inductive reactance of $30\ \Omega$ and a capacitor with a capacitive reactance of $40\ \Omega$, all connected across a $120\text{ V}/60\text{ Hz}$ supply. Answer the questions that follow.

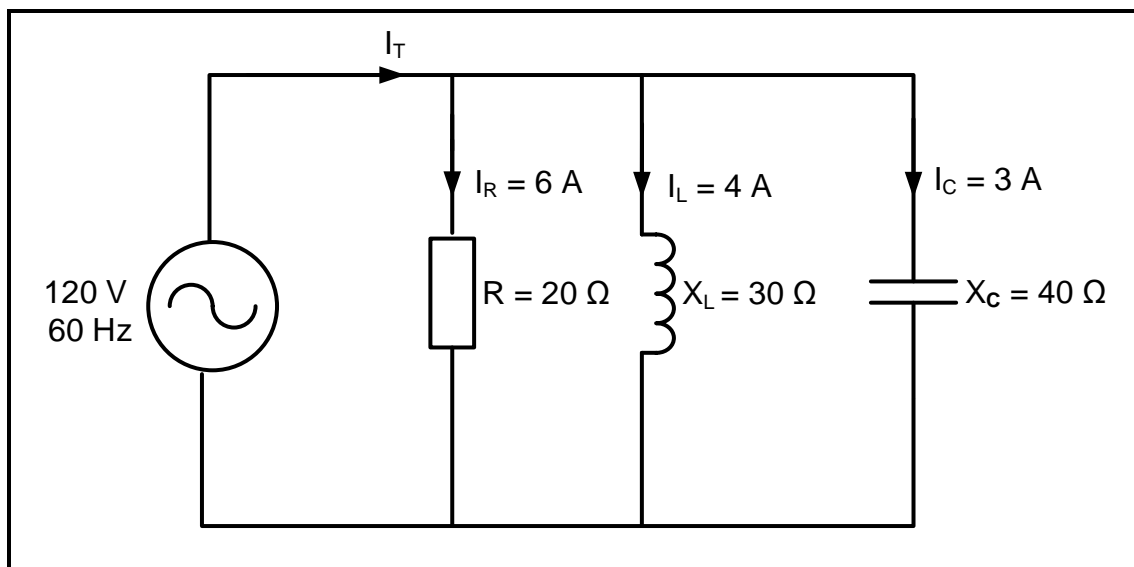


FIGURE 2.4: RLC PARALLEL CIRCUIT

Given:

$$\begin{aligned} R &= 20\ \Omega \\ X_L &= 30\ \Omega \\ X_C &= 40\ \Omega \\ V_T &= 120\text{ V} \\ f &= 60\text{ Hz} \end{aligned}$$

- 2.4.1 Calculate the total current in the circuit. (3)
- 2.4.2 Calculate the phase angle. (3)
- 2.4.3 State whether the phase angle is leading or lagging. Motivate your answer. (2)

- 2.5 FIGURE 2.5 below shows an RLC series resonant circuit which consists of a $12\ \Omega$ resistor, an inductor with an inductive reactance of $50\ \Omega$ and a variable capacitor, all connected across a $120\text{ V}/2\text{ kHz}$ supply. Answer the questions that follow.

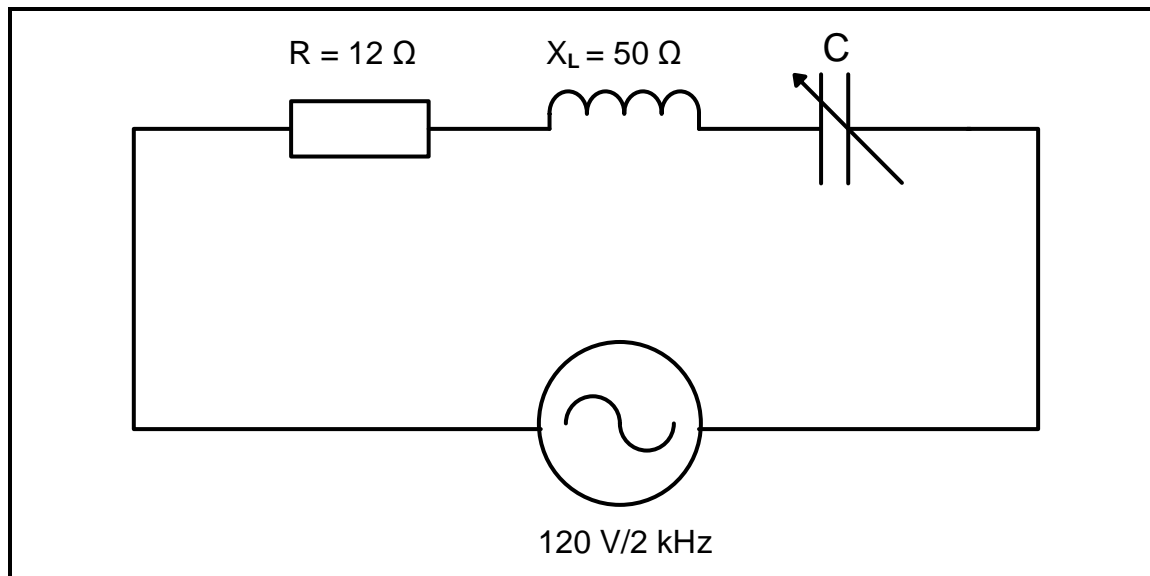


FIGURE 2.5: RLC SERIES RESONANT CIRCUIT


Given:

$$\begin{aligned}V_T &= 120\text{ V} \\f &= 2\text{ kHz} \\R &= 12\ \Omega \\X_L &= 50\ \Omega\end{aligned}$$


- 2.5.1 Calculate the value of **C** when the circuit resonates at 2 kHz. (4)
- 2.5.2 Calculate the value of the current in the circuit. (4)
- 2.5.3 State how current will be affected if the value of the resistance is doubled. (1)
- 2.5.4 List THREE characteristics of an RLC series circuit at resonance. (3)
- [40]**

QUESTION 3: SEMICONDUCTOR DEVICES

- 3.1 Name the type of material used for the gate terminal in a P-channel JFET. (1)
- 3.2 Draw a neatly labelled symbol of an N-channel JFET. (3)
- 3.3 Study the symbol in FIGURE 3.3 below and answer the questions that follow.

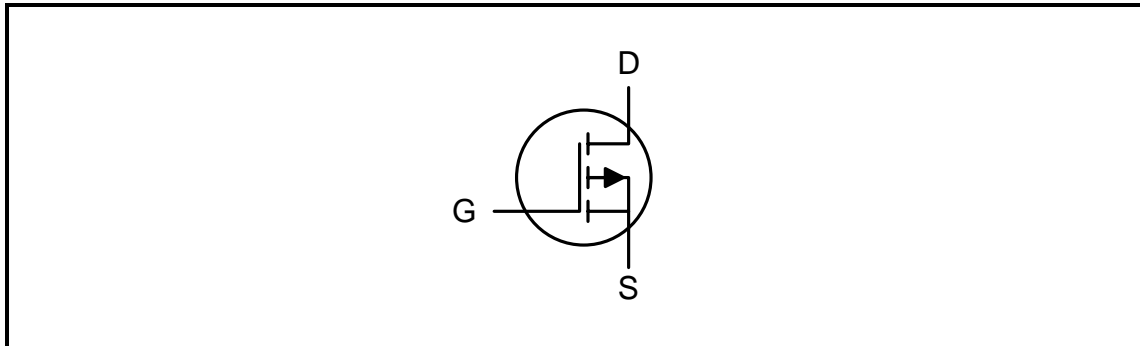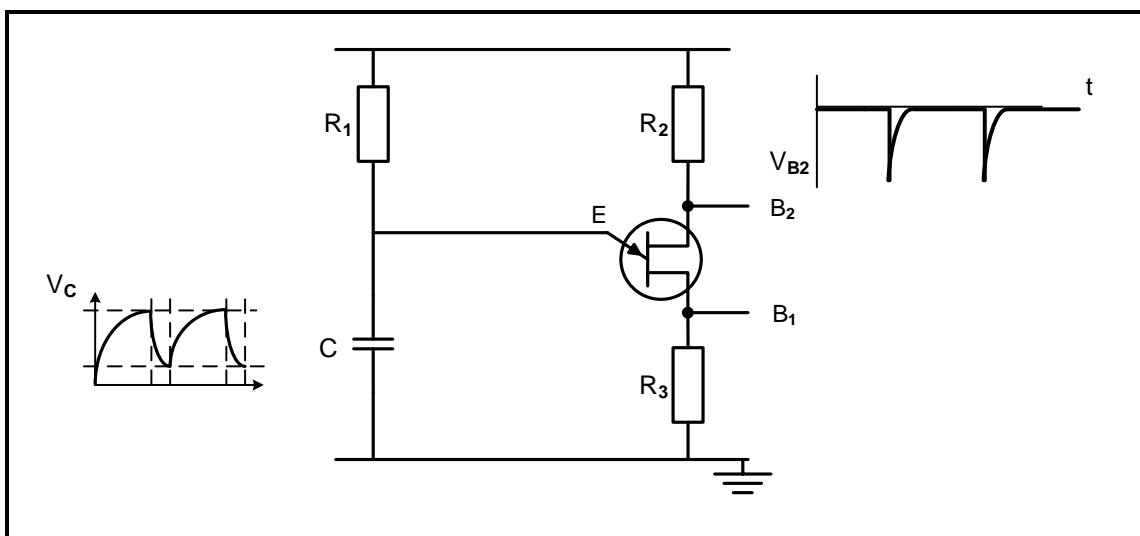**FIGURE 3.3: FIELD-EFFECT TRANSISTOR**

- 3.3.1 State whether the field-effect transistor (FET) in FIGURE 3.3 is a P-channel or an N-channel. (1)
- 3.3.2 List THREE conditions for the correct biasing of the transistor in FIGURE 3.3. (3)
- 3.4 Refer to FIGURE 3.4 below and answer the questions that follow.

**FIGURE 3.4: UJT AS A SAWTOOTH GENERATOR**

- 3.4.1 Besides a sawtooth generator, name ONE other application of a UJT. (1)
- 3.4.2 Explain what causes the UJT to trigger ON in the circuit. (2)
- 3.4.3 Draw the output waveform between points B₁ and ground on the ANSWER SHEET for QUESTION 3.4.3. (3)

3.5 Refer to FIGURE 3.5 below and answer the questions that follow.

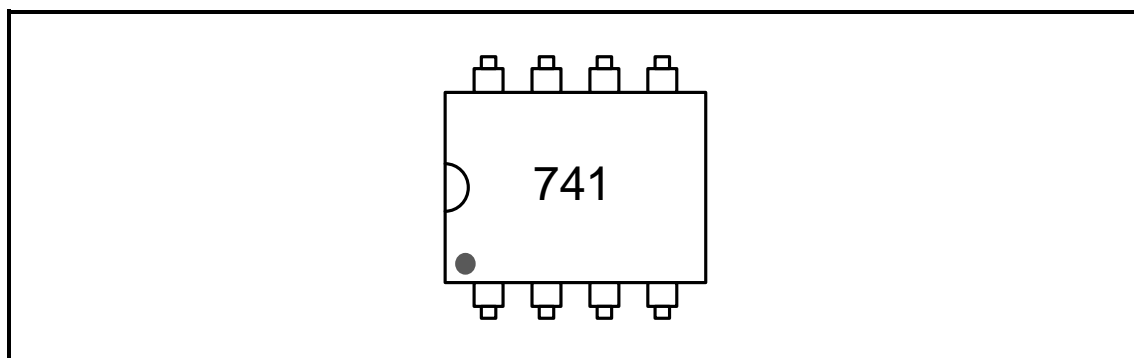


FIGURE 3.5: 741 OP-AMP

3.5.1 State how you would identify pin 1 of the IC in FIGURE 3.5. (1)

3.5.2 List the THREE stages into which the internal circuit of the op-amp is divided. (3)

3.6 FIGURE 3.6 below shows the op-amp as an inverting amplifier. Answer the questions that follow.

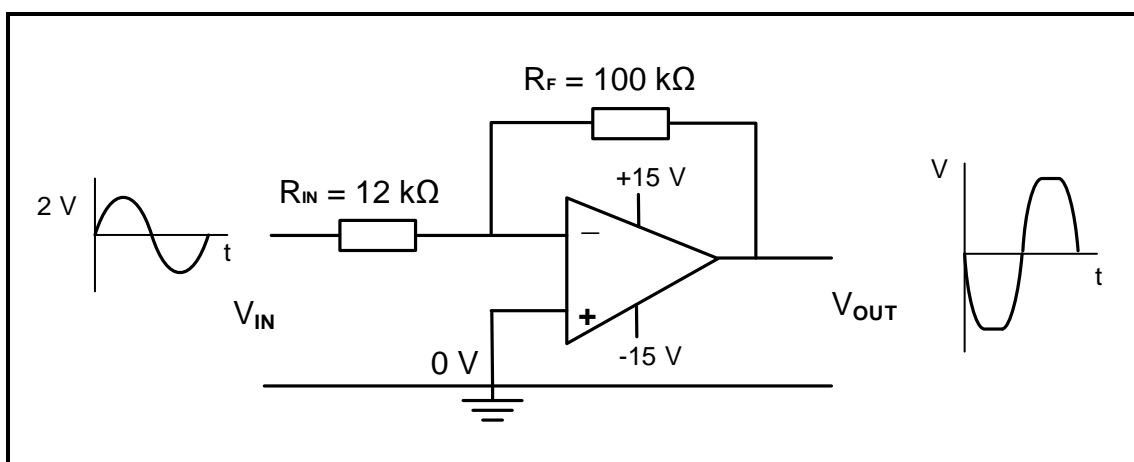


FIGURE 3.6: INVERTING OP-AMP

Given:

$$\begin{aligned} V_{IN} &= 2 \text{ V} \\ R_F &= 100 \text{ k}\Omega \\ R_{IN} &= 12 \text{ k}\Omega \end{aligned}$$

3.6.1 Calculate the output voltage based on the data in FIGURE 3.6. (3)

3.6.2 Explain why the shape of the output waveform is NOT an exact replica of the input waveform. (2)

3.6.3 Identify the maximum output voltages (V_{out}). (2)

- 3.7 Refer to the data sheet in FIGURE 3.7 below and answer the questions that follow.

N DIP8

OPERATING CONDITIONS

Symbol	Parameter	Value	Unit
V_{CC}	Supply Voltage NE555 SA555 SE555	4.5 to 16 4.5 to 16 4.5 to 18	V
$V_{th}, V_{trig}, V_{cl}, V_{reset}$	Maximum Input Voltage	V_{CC}	V
T_{oper}	Operating Free Air Temperature Range for NE555 for SA555 for SE555	0 to 70 -40 to 105 -55 to 125	°C

ELECTRICAL CHARACTERISTICS $T_{amb} = +25^{\circ}\text{C}$, $V_{CC} = +5\text{V}$ to $+15\text{V}$ (unless otherwise specified)

Symbol	Parameter	SE555			NE555 - SA555			Unit
		Min.	Typ.	Max.	Min.	Typ.	Max.	
I_{CC}	Supply Current ($R_L = \infty$) - note ¹ Low State $V_{CC} = +5\text{V}$ $V_{CC} = +15\text{V}$ High State $V_{CC} = 5\text{V}$		3 10 2	5 12		3 10 2	6 15	mA
	Timing Error (monostable) ($R_A = 2\text{k}\Omega$ to $100\text{k}\Omega$, $C = 0.1\mu\text{F}$) Initial Accuracy - note ² Drift with Temperature Drift with Supply Voltage		0.5 30 0.05	2 100 0.2		1 50 0.1	3 150 0.5	% ppm/°C %/V
	Timing Error (astable) ($R_A, R_B = 1\text{k}\Omega$ to $100\text{k}\Omega$, $C = 0.1\mu\text{F}$, $V_{CC} = +15\text{V}$) Initial Accuracy - see note ² Drift with Temperature Drift with Supply Voltage		1.5 90 0.15			2.25 150 0.3		% ppm/°C %/V
V_{CL}	Control Voltage Level $V_{CC} = +15\text{V}$ $V_{CC} = +5\text{V}$	9.6 2.9	10 3.33	10.4 3.8	9 2.6	10 3.33	11 4	V
V_{th}	Threshold Voltage $V_{CC} = +15\text{V}$ $V_{CC} = +5\text{V}$	9.4 2.7	10 3.33	10.6 4	8.8 2.4	10 3.33	11.2 4.2	V
I_{th}	Threshold Current - note ³		0.1	0.25		0.1	0.25	μA
V_{trig}	Trigger Voltage $V_{CC} = +15\text{V}$ $V_{CC} = +5\text{V}$	4.8 1.45	5 1.67	5.2 1.9	4.5 1.1	5 1.67	5.6 2.2	V


FIGURE 3.7: DATA SHEET

- 3.7.1 Rewrite the abbreviation *DIP* in full. (1)
- 3.7.2 Write down the maximum supply voltage for the NE555 IC. (1)
- 3.7.3 Identify the typical trigger voltage of the NE555 IC, in the data sheet above, when the supply voltage is +15 V. (1)
- 3.8 Explain what will happen to the output of an NE555 IC when the trigger voltage rises above the threshold voltage level of 10 V. (2)

[30]

QUESTION 4: SWITCHING CIRCUITS


4.1 Refer to FIGURE 4.1 below and answer the questions that follow.

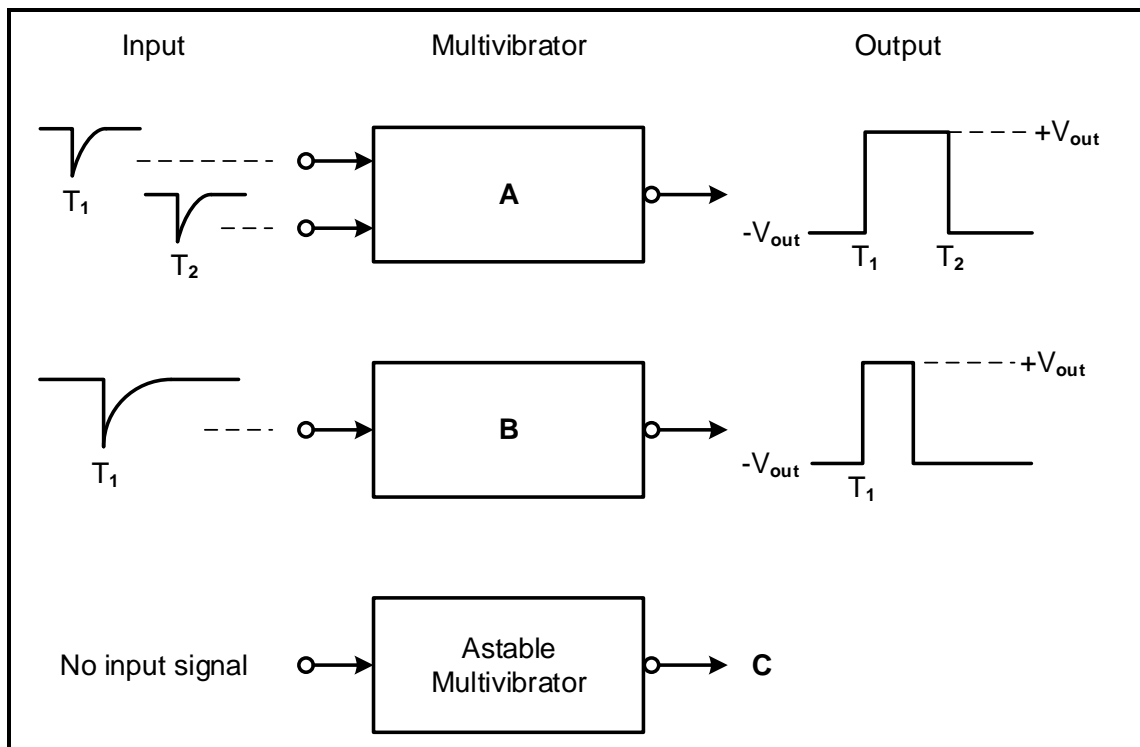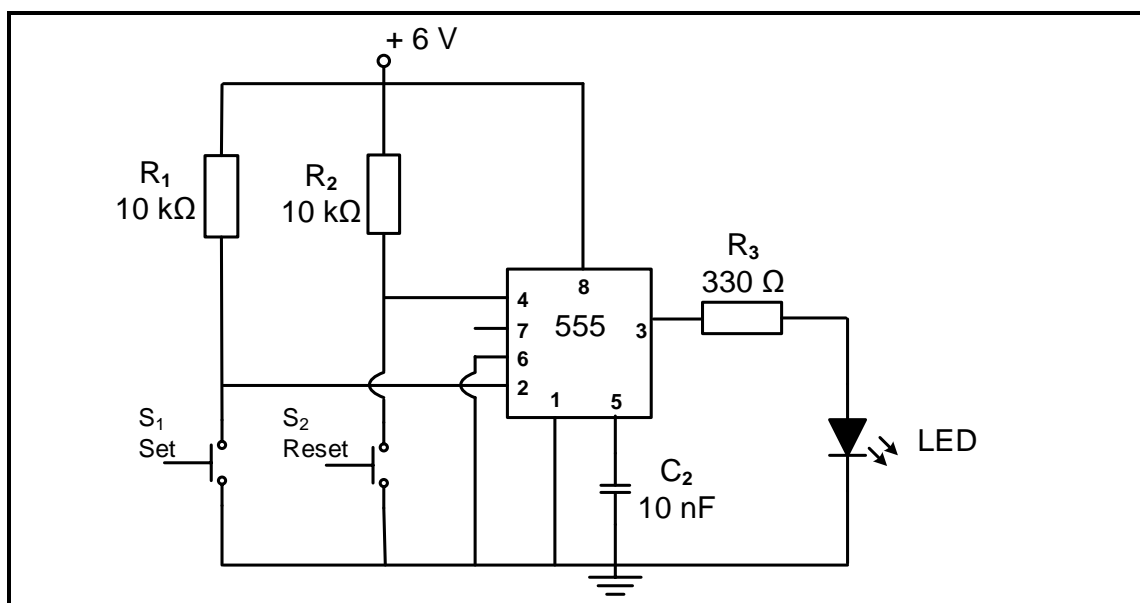**FIGURE 4.1: MULTIVIBRATORS**

4.1.1 Identify multivibrators **A** and **B**. (2)

4.1.2 Draw the output signal of the astable multivibrator at **C** on the ANSWER SHEET for QUESTION 4.1.2. (2)

4.2 Refer to the circuit in FIGURE 4.2 below and answer the questions that follow.

**FIGURE 4.2: BISTABLE MULTIVIBRATOR**

4.2.1 State the function of R_1 and R_2 . (2)

4.2.2 Describe what happens when the set switch, S_1 , is pressed. (3)

4.2.3 Explain why threshold pin 6 is connected directly to ground. (3)

4.3 Refer to FIGURE 4.3 below and answer the questions that follow.

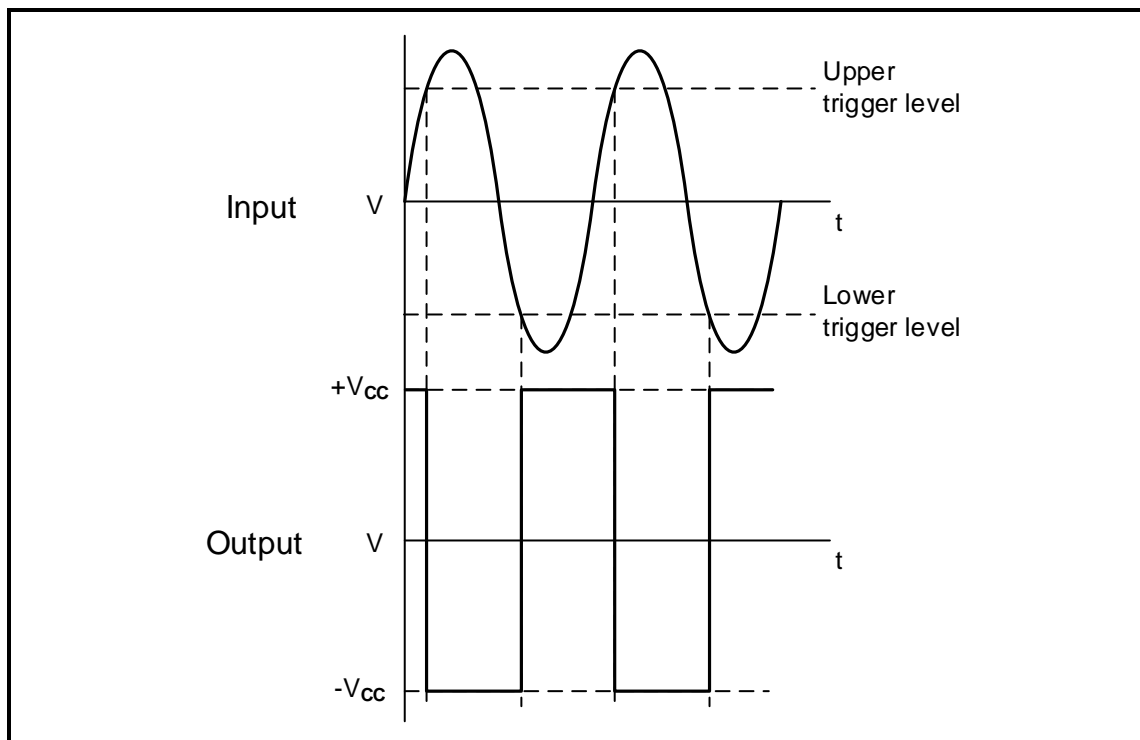


FIGURE 4.3: SCHMITT TRIGGER INPUT AND OUTPUT

- 4.3.1 State whether the output signal represents an inverting or a non-inverting Schmitt trigger. Motivate your answer. (3)
- 4.3.2 Draw the circuit diagram of the Schmitt trigger consisting of two resistors and a 741 op-amp that will produce the output signal in FIGURE 4.3. (7)

4.4 Refer to FIGURE 4.4 below and answer the questions that follow.

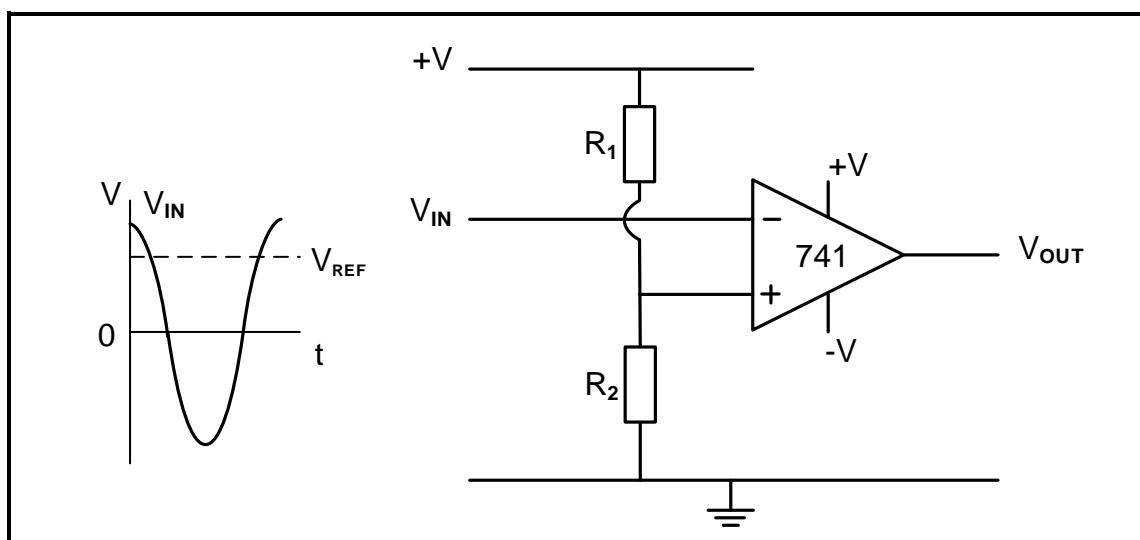


FIGURE 4.4: OP-AMP CIRCUIT DIAGRAM

- 4.4.1 Identify the op-amp circuit diagram in FIGURE 4.4. (2)
- 4.4.2 Draw the output signal on the ANSWER SHEET for QUESTION 4.4.2 (4)
- 4.4.3 Explain how the reference voltage is made negative. (2)

4.5 Refer to FIGURE 4.5 below and answer the questions that follow.

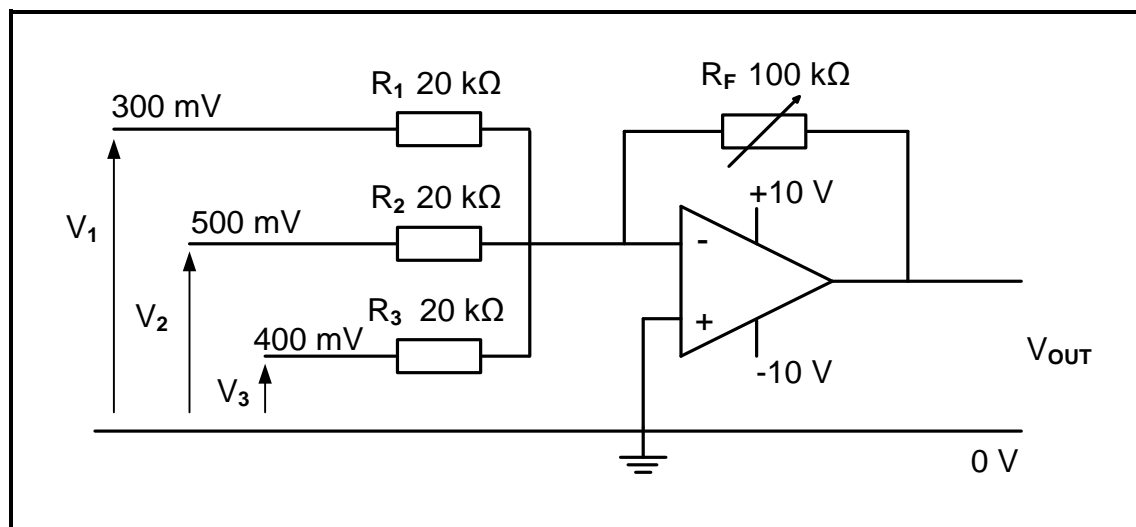


FIGURE 4.5: INVERTING SUMMING AMPLIFIER

Given:

$$\begin{aligned} V_1 &= 300 \text{ mV} \\ V_2 &= 500 \text{ mV} \\ V_3 &= 400 \text{ mV} \\ R_F &= 100 \text{ k}\Omega \end{aligned}$$

$$R_1 = R_2 = R_3 = 20 \text{ k}\Omega$$

- 4.5.1 Explain how the gain of this amplifier can be determined. (3)
- 4.5.2 Calculate the output voltage of the amplifier. (3)
- 4.5.3 Give a reason why the amplifier is NOT saturated. (2)
- 4.5.4 Calculate the gain of the amplifier using voltage values. (3)
- 4.5.5 Explain the advantage of using a variable resistor in the feedback loop instead of a fixed resistor. (2)
- 4.5.6 Describe what will happen to the output voltage if the value of R_2 is changed to $10 \text{ k}\Omega$. (2)

4.6 Refer to FIGURE 4.6 below and answer the questions that follow.

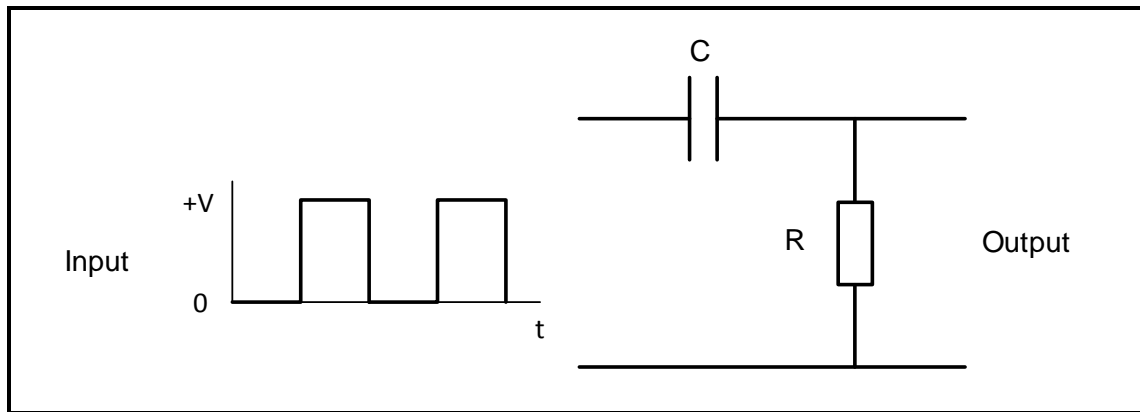


FIGURE 4.6: CIRCUIT DIAGRAM

- 4.6.1 Identify the circuit diagram in FIGURE 4.6. (2)
- 4.6.2 Draw the output signal on the ANSWER SHEET for QUESTION 4.6.2 for the given circuit time constant. (3)
- 4.6.3 Explain how the output will be affected if the circuit time constant is increased. (2)

4.7 Refer to FIGURE 4.7 below and answer the questions that follow.

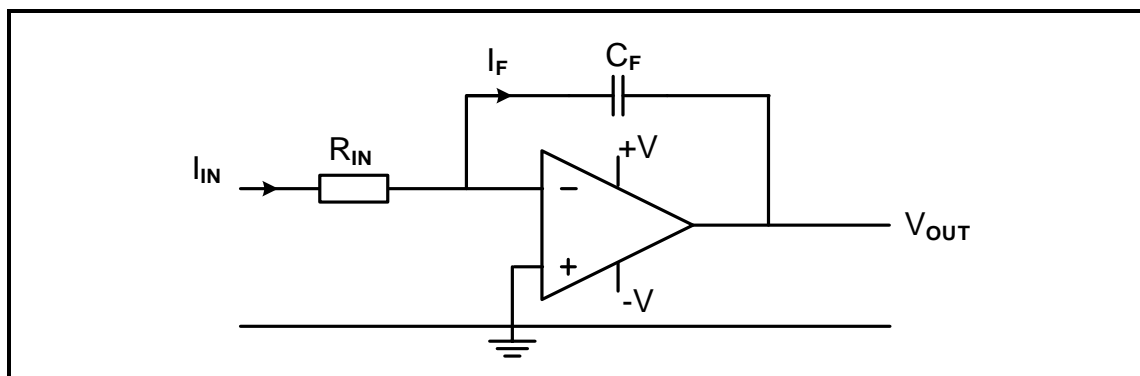


FIGURE 4.7: OP-AMP AS INVERTING INTEGRATOR

- 4.7.1 State the purpose of C_F . (1)
- 4.7.2 Name THREE key operating points of the circuit in FIGURE 4.7. (3)
- 4.7.3 Draw the output signal on the ANSWER SHEET for QUESTION 4.7.3 if the signal below is applied to the input. (4)

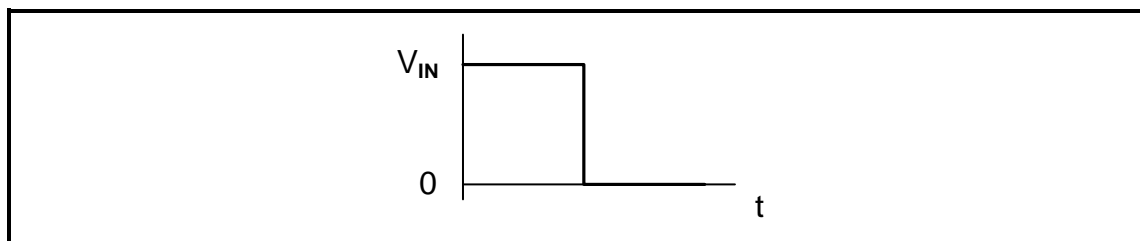


FIGURE 4.7.3: APPLIED SIGNAL

(4)
[60]

QUESTION 5: AMPLIFIERS

5.1 Compare Class A and Class B amplifiers with reference to the following:

5.1.1 Q-point (2)

5.1.2 Efficiency (2)

5.2 Refer to FIGURE 5.2 below and answer the questions that follow.

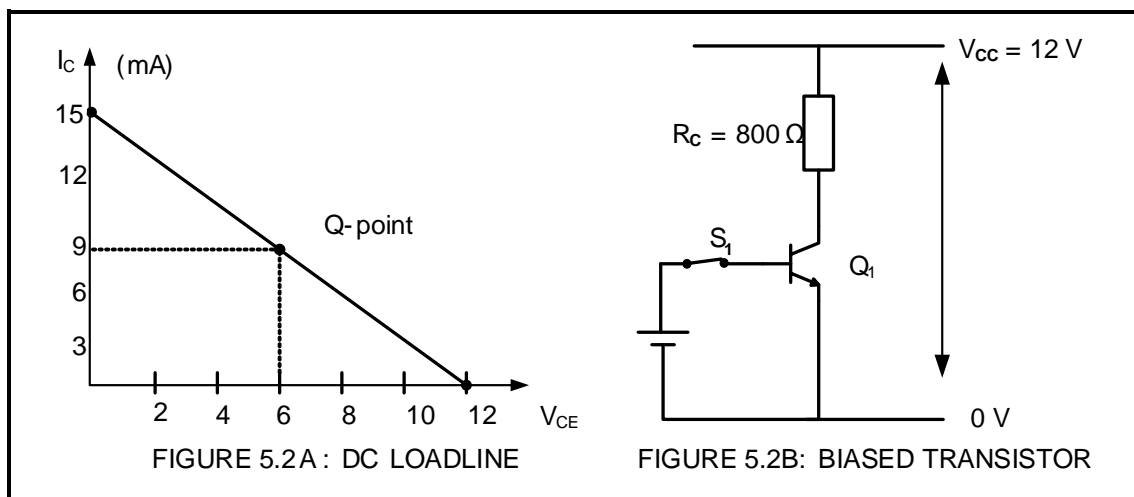


FIGURE 5.2: TRANSISTOR AMPLIFIER

5.2.1 State ONE function of the collector resistor in FIGURE 5.2B. (1)

5.2.2 Explain how V_{CE} becomes equivalent to V_{CC} when S_1 is open. (2)

5.3 With reference to biasing, explain *Class C amplification*. (2)

5.4 Refer to FIGURE 5.4 below and draw the output waveforms on the ANSWER SHEET for QUESTION 5.4 when the transistor is operating as the following:

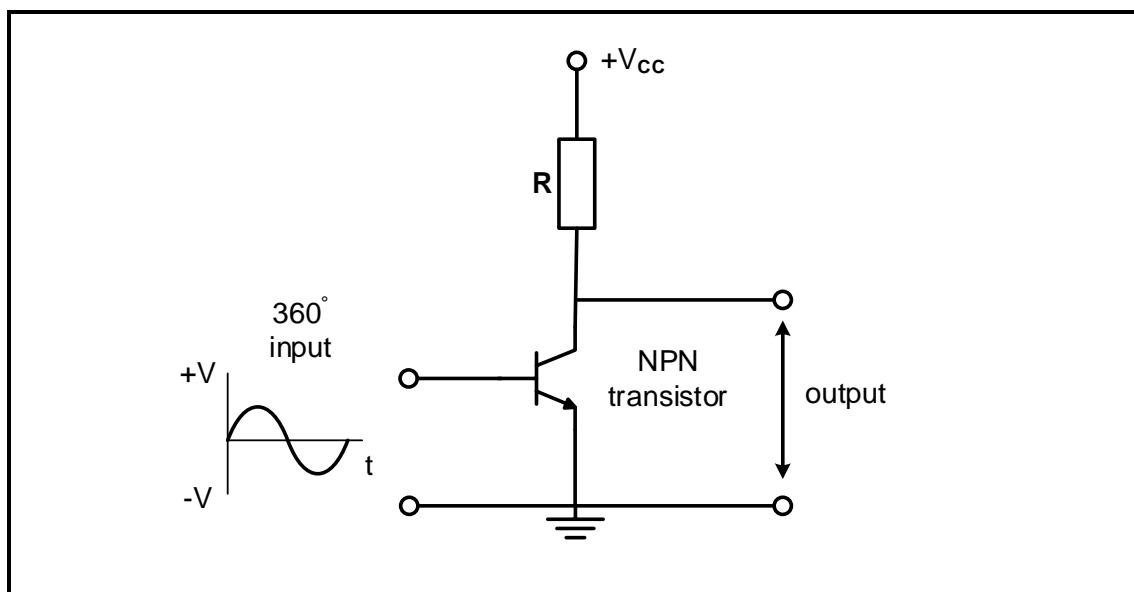


FIGURE 5.4: BIASED NPN TRANSISTOR

5.4.1 Class A amplifier (3)

5.4.2 Class AB amplifier (3)

- 5.5 State ONE undesirable condition that may occur due to the incorrect biasing of a transistor. (1)
- 5.6 Refer to FIGURE 5.6 below and answer the questions that follow.

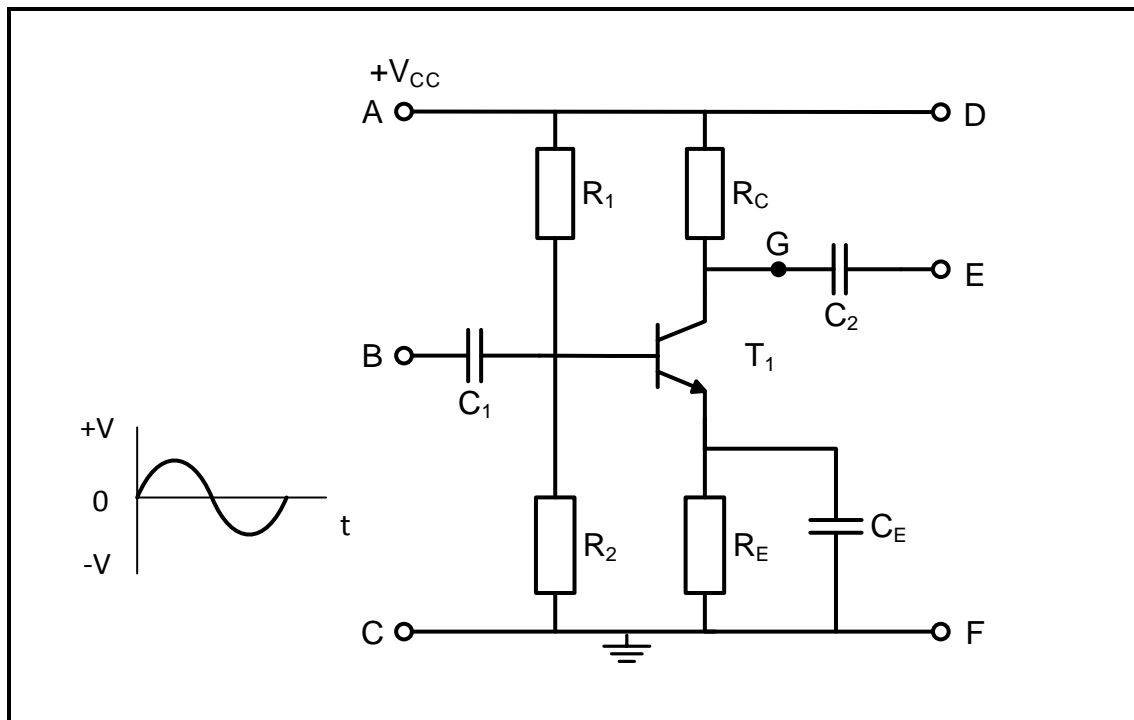


FIGURE 5.6: COMMON EMITTER AMPLIFIER

- 5.6.1 Explain why the circuit is called a common emitter amplifier. (2)
- 5.6.2 Name the points where the input signal and the load will be connected. (2)
- 5.6.3 Identify the TWO components that protect the transistor from thermal runaway. (2)
- 5.6.4 Draw the waveform that would appear between points **G** and **F** on the ANSWER SHEET for QUESTION 5.6.4. (3)
- 5.6.5 Draw the output waveform that would appear between points **E** and **F** on the ANSWER SHEET for QUESTION 5.6.5. (3)
- 5.7 Give TWO reasons for using coupling methods in amplifier circuits. (2)

5.8 A push-pull amplifier circuit has the following information:

Given:

Input power = 3 015 watts
 Output power = 1 200 watts
 Input voltage = 230 V
 Output voltage = 219 V
 Output current = 5,48 A
 Output impedance = 40 Ω

Calculate the following:

5.8.1 Power gain in dB (3)

5.8.2 Voltage gain in dB (3)

5.9 Define the term *gain* of an amplifier. (2)

5.10 A certain cascaded amplifier (three-stage amplifier) arrangement has the following voltage gain:
 $A_{V1} = 10$, $A_{V2} = 15$ and $A_{V3} = 20$.
 Calculate the total voltage gain. (3)

5.11 Refer to the amplifier circuit diagram in FIGURE 5.11 below and answer the questions that follow.

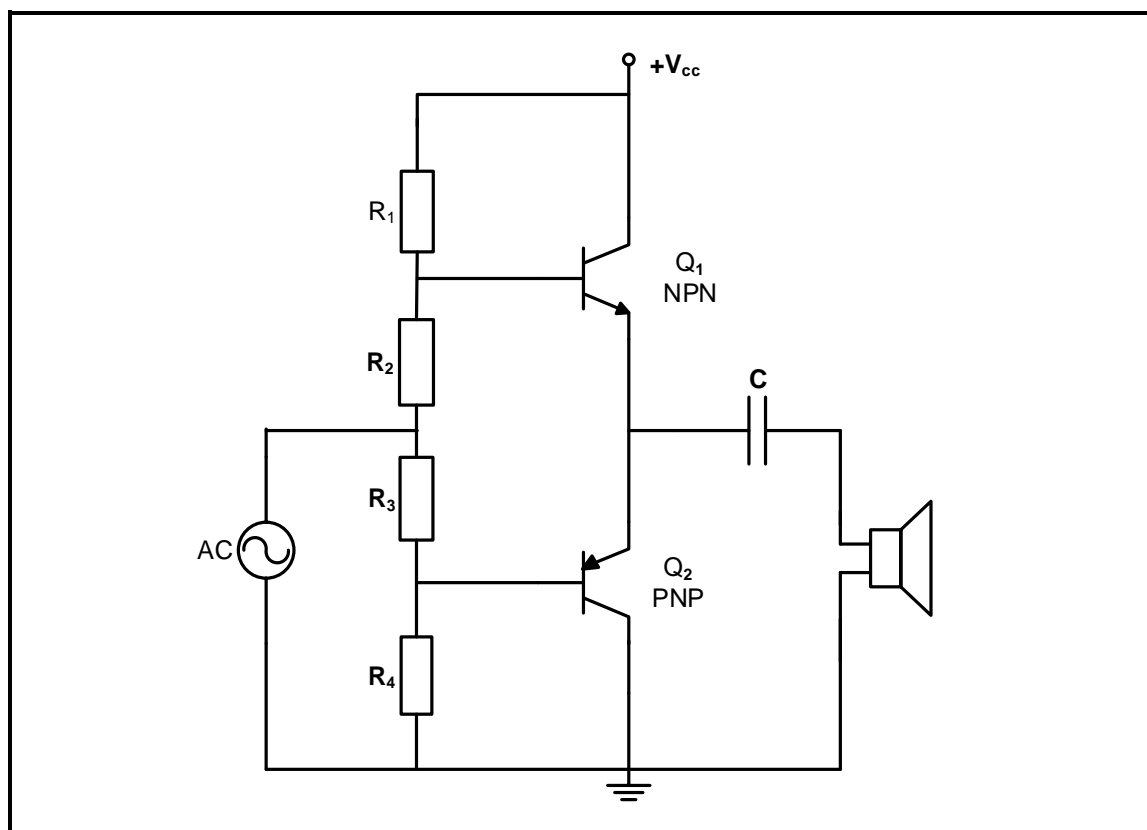


FIGURE 5.11: AMPLIFIER CIRCUIT DIAGRAM

5.11.1 Identify the circuit diagram in FIGURE 5.11. (2)

5.11.2 Explain how cross-over distortion is eliminated in this amplifier. (2)

5.11.3 State the purpose of the resistors in the circuit diagram. (1)

5.11.4 Draw a fully labelled output waveform of the circuit diagram on the ANSWER SHEET for QUESTION 5.11.4. (3)

- 5.12 FIGURE 5.12 below shows an FET oscillator circuit diagram. Answer the questions that follow.

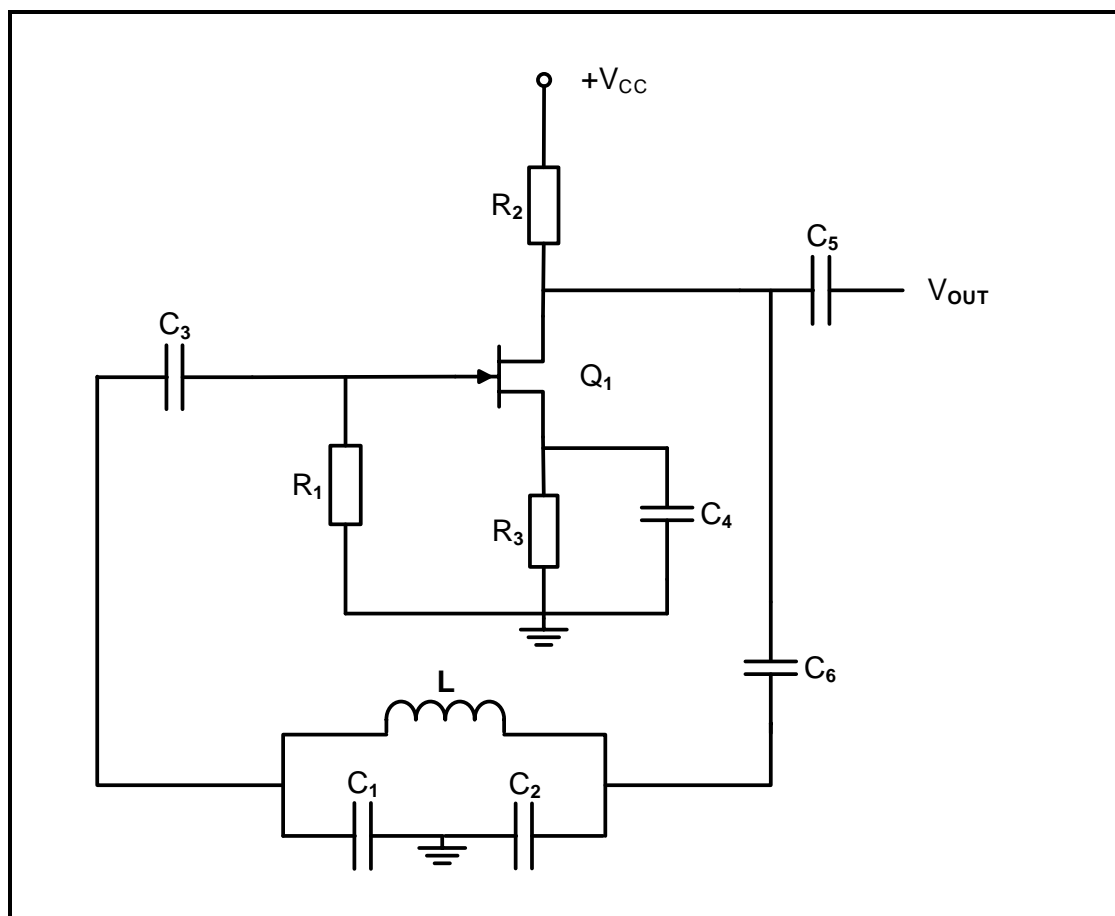


FIGURE 5.12: COLPITTS OSCILLATOR USING FET TRANSISTOR

Compare the differences between RC and LC oscillators with reference to the following:

- 5.12.1 Feedback circuit (2)
- 5.12.2 Oscillation frequency (2)
- 5.13 Draw a modified tank circuit to change the Colpitts oscillator in FIGURE 5.12 into a Hartley oscillator. (3)
- 5.14 Name TWO functions of transistor Q_1 in FIGURE 5.12. (2)
- 5.15 Name TWO similarities between an LC oscillator and an RC oscillator. (2)

[60]

TOTAL: 200

FORMULA SHEET	
RLC CIRCUITS	SEMICONDUCTOR DEVICES
$P = V \times I \times \cos \theta$ $X_L = 2\pi fL$ $X_C = \frac{1}{2\pi fC}$ $f_r = \frac{1}{2\pi\sqrt{LC}}$ $BW = \frac{f_r}{Q}$ Series $V_R = IR$ $V_L = IX_L$ $V_C = IX_C$ $I_T = \frac{V_T}{Z} \quad \text{OR} \quad I_T = I_R = I_C = I_L$ $Z = \sqrt{R^2 + (X_L - X_C)^2}$ $V_T = \sqrt{V_R^2 + (V_L - V_C)^2} \quad \text{OR} \quad V_T = IZ$ $\cos \theta = \frac{R}{Z} \quad \text{OR} \quad \cos \theta = \frac{V_R}{V_T}$ $Q = \frac{X_L}{Z} = \frac{X_C}{Z} = \frac{V_L}{V_T} = \frac{V_C}{V_T} = \frac{1}{R} \sqrt{\frac{L}{C}}$ Parallel $V_T = V_R = V_L = V_C$ $I_R = \frac{V_T}{R}$ $I_C = \frac{V_T}{X_C}$ $I_L = \frac{V_T}{X_L}$ $I_T = \sqrt{I_R^2 + (I_L - I_C)^2}$ $Z = \frac{V_T}{I_T}$ $\cos \theta = \frac{I_R}{I_T}$ $Q = \frac{X_L}{Z} = \frac{X_C}{Z} = \frac{I_L}{I_T} = \frac{I_C}{I_T} = \frac{1}{R} \sqrt{\frac{L}{C}}$	$\text{Gain } A_V = \frac{V_{OUT}}{V_{IN}} = - \left(\frac{R_F}{R_{IN}} \right)$ $V_{OUT} = V_{IN} \times \left(- \frac{R_F}{R_{IN}} \right)$ $V_{OUT} = V_{IN} \times \left(1 + \frac{R_F}{R_{IN}} \right)$ SWITCHING CIRCUITS $V_{OUT} = - \left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + \dots V_N \frac{R_F}{R_N} \right)$ $\text{Gain } A_V = \frac{V_{OUT}}{V_{IN}} = \frac{V_{OUT}}{(V_1 + V_2 + \dots V_N)}$ $V_{OUT} = -(V_1 + V_2 + \dots V_N)$ AMPLIFIERS $I_C = \frac{V_C}{R_C}$ $V_{CC} = V_{CE} + I_C R_C$ $A_V = \frac{V_{OUT}}{V_{IN}}$ $A_I = \frac{I_{OUT}}{I_{IN}}$ $A = \beta_1 \times \beta_2 \quad \text{OR} \quad A_V = A_{V1} \times A_{V2} \times A_{V3}$ $P_{IN} = I^2 \times Z_{IN}$ $P_{OUT} = I^2 \times Z_{OUT}$ GAIN IN DECIBELS $A_I = 20 \log_{10} \frac{I_{OUT}}{I_{IN}}$ $A_V = 20 \log_{10} \frac{V_{OUT}}{V_{IN}}$ $A_P = 10 \log_{10} \frac{P_{OUT}}{P_{IN}}$


CENTRE NUMBER:

EXAMINATION NUMBER:

ANSWER SHEET

QUESTION 2: RLC CIRCUITS

2.3.4

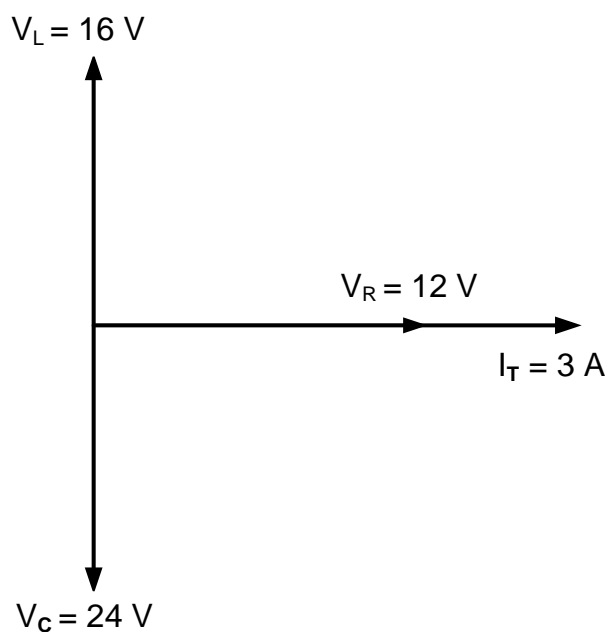Transfer mark to
answer book

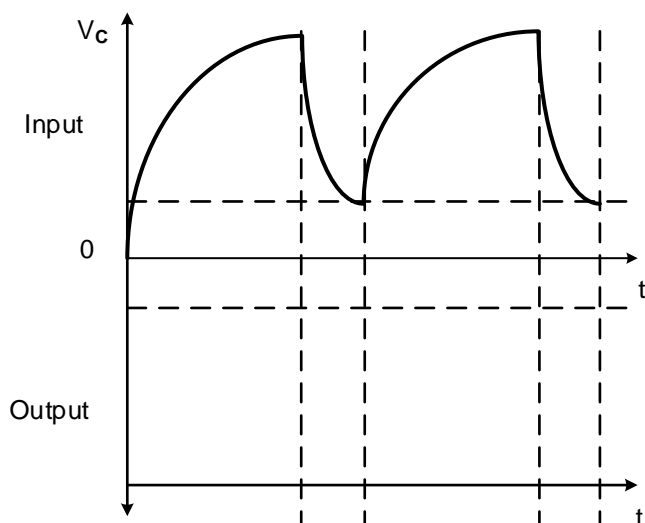
MOD

FIGURE 2.3.4

(4)

QUESTION 3: SEMICONDUCTOR DEVICES

3.4.3

Transfer mark to
answer book

MOD

FIGURE 3.4.3

(3)


CENTRE NUMBER:

EXAMINATION NUMBER:

ANSWER SHEET

QUESTION 4: SWITCHING CIRCUITS

4.1.2

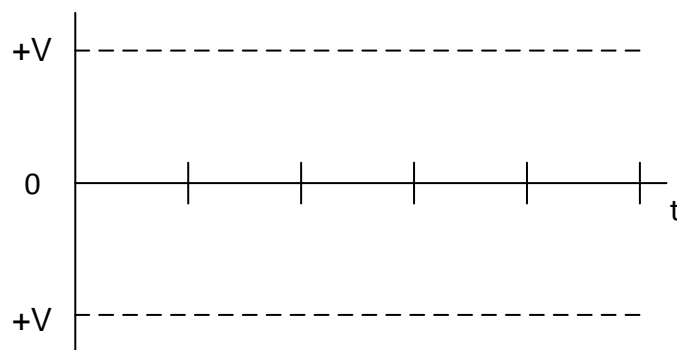
Transfer mark to
answer book

MOD

FIGURE 4.1.2

(2)

4.4.2

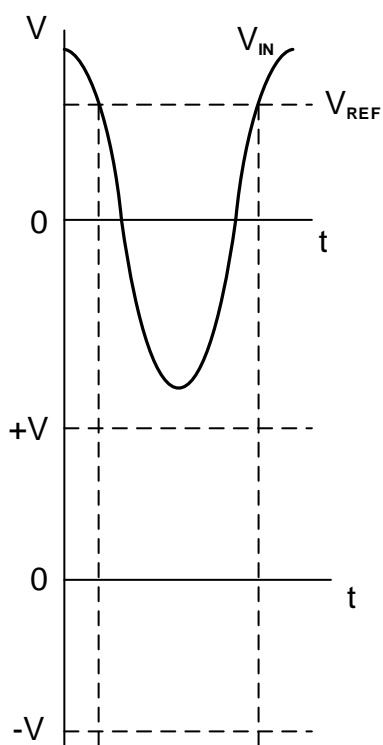Transfer mark to
answer book

MOD

FIGURE 4.4.2

(4)

CENTRE NUMBER:

EXAMINATION NUMBER:

ANSWER SHEET

4.6.2

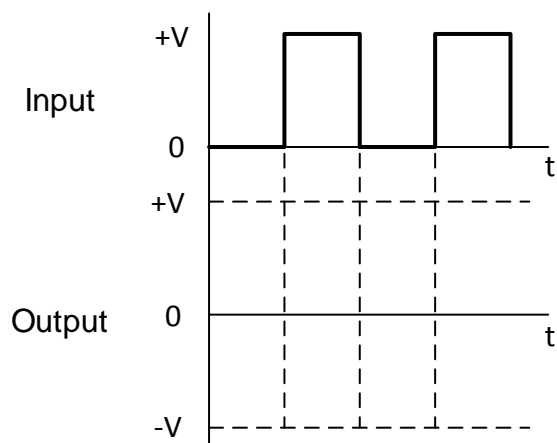


FIGURE 4.6.2

Transfer mark to
answer book

MOD

(3)

4.7.3

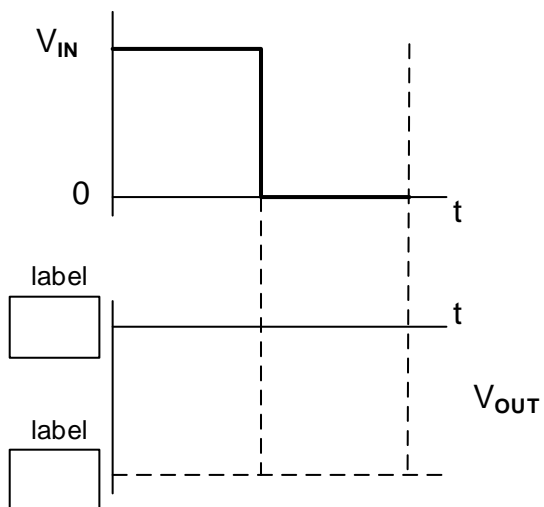
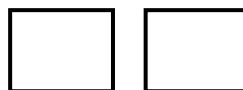


FIGURE 4.7.3

Transfer mark to
answer book

MOD


(4)

CENTRE NUMBER:								
----------------	--	--	--	--	--	--	--	--

EXAMINATION NUMBER:													
---------------------	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET**QUESTION 5: AMPLIFIERS**


5.4.1

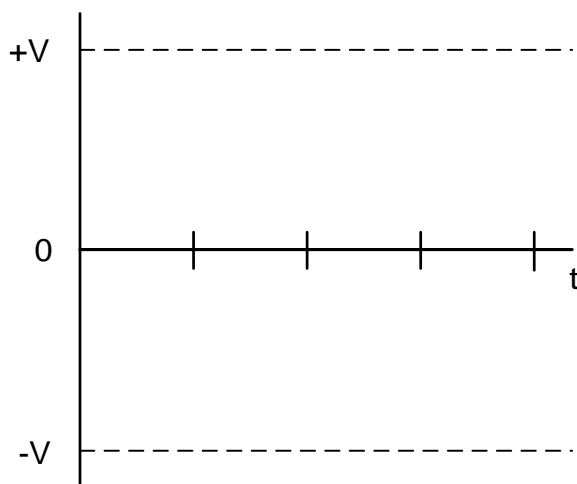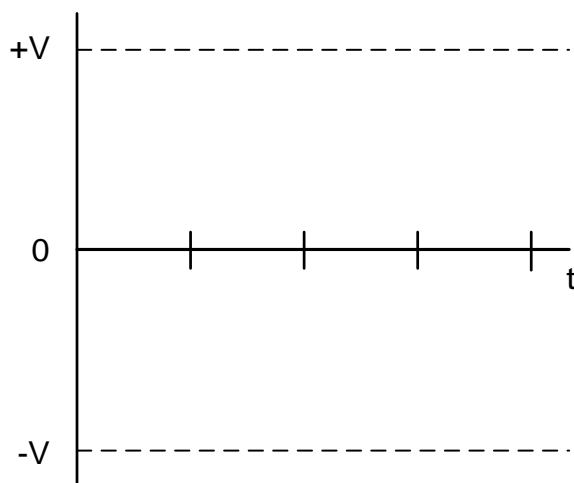**FIGURE 5.4.1**Transfer mark to
answer book

MOD

(3)

5.4.2

**FIGURE 5.4.2**Transfer mark to
answer book

MOD


(3)

CENTRE NUMBER:									
----------------	--	--	--	--	--	--	--	--	--

EXAMINATION NUMBER:														
---------------------	--	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET


5.6.4

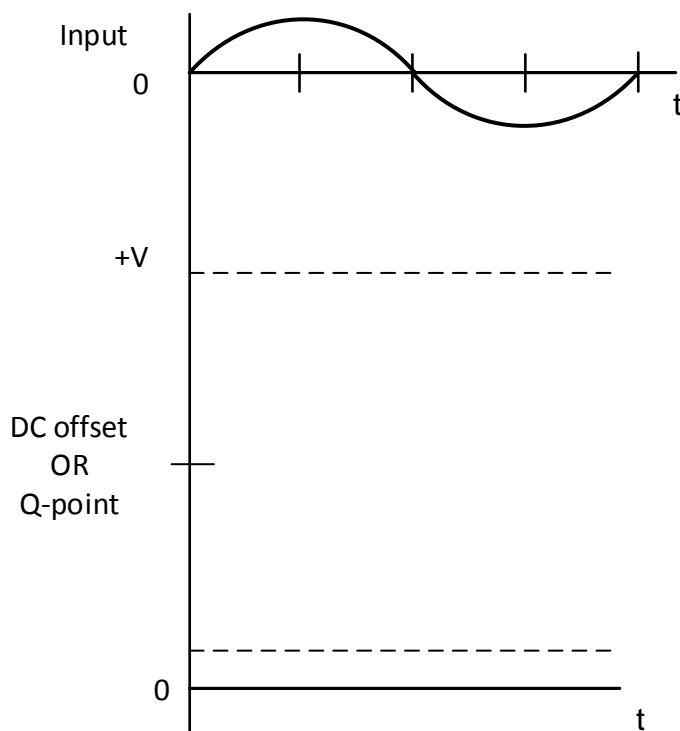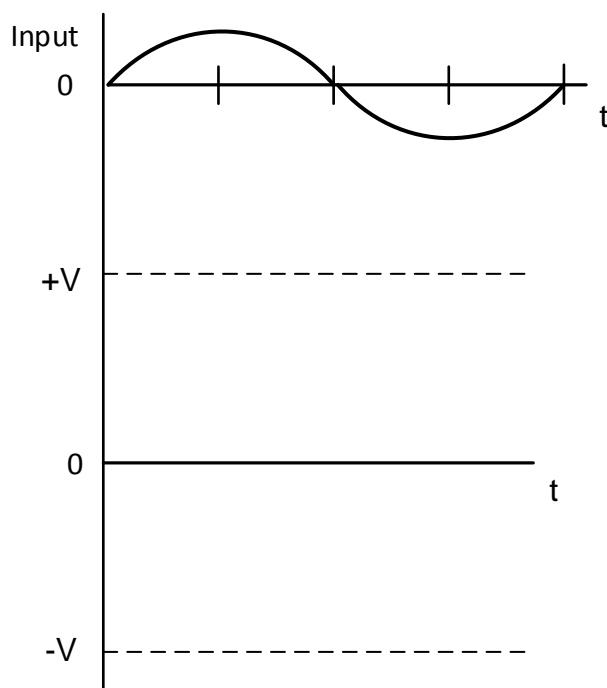**FIGURE 5.6.4**Transfer mark to
answer book

MOD

(3)

5.6.5

**FIGURE 5.6.5**Transfer mark to
answer book

MOD


(3)

CENTRE NUMBER:								
----------------	--	--	--	--	--	--	--	--

EXAMINATION NUMBER:													
---------------------	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET

5.11.4

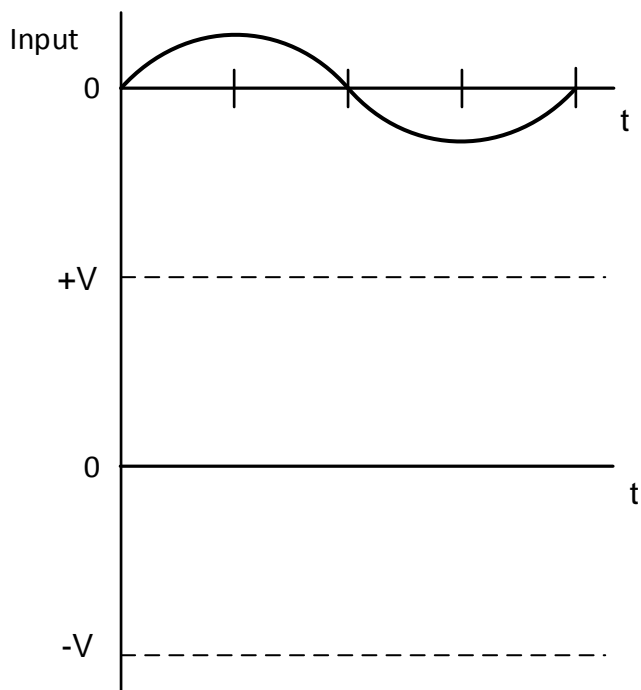**FIGURE 5.11.4**Transfer mark to
answer book

MOD

(3)