

You have Downloaded, yet Another Great Resource to assist you with your Studies ③

Thank You for Supporting SA Exam Papers

Your Leading Past Year Exam Paper Resource Portal

Visit us @ www.saexampapers.co.za







NATIONAL SENIOR CERTIFICATE

GRADE 12

SEPTEMBER 2022

ELECTRICAL TECHNOLOGY: ELECTRONICS MARKING GUIDELINE

MARKS: 200

This marking guideline consists of 11 pages.

INSTRUCTIONS TO MARKERS

- 1. All calculations with multiple answers imply that any relevant, acceptable answer should be considered.
- 2. Calculations:
 - 2.1 All calculations must show the formulae.
 - 2.2 Substitution of values must be done correctly.
 - 2.3 All answers MUST contain the correct unit to be considered.
 - 2.4 Alternative methods must be considered, provided that the correct answer is obtained.
 - 2.5 Where an incorrect answer could be carried over to the next step, the first answer will be deemed incorrect. However, should the incorrect answer be carried over correctly, the marker has to re-calculate the values, using the incorrect answer from the first calculation. If correctly used, the candidate should receive the full marks for subsequent calculations.
 - 2.6 Markers should consider that learners answers may deviate slightly from the marking guideline depending on how and where in the calculation rounding off was used.
- 3. These marking guidelines are only a guide with model answers.
- 4. Alternative interpretations must be considered and marked on merit. However, this principle should be applied consistently throughout the marking session at ALL marking centres.

QUESTION 1: MULTIPLE CHOICE-QUESTIONS

1.1	A✓	(1)
1.2	C√	(1)
1.3	B√	(1)
1.4	C√	(1)
1.5	B√	(1)
1.6	B√	(1)
1.7	C✓	(1)
1.8	D√	(1)
1.9	B√	(1)
1.10	A✓	(1)
1.11	C√	(1)
1.12	A✓	(1)
1.13	A✓	(1)
1.14	A✓	(1)
1.15	A✓	(1)
		[15]

QUESTION 2: OCCUPATIONAL HEALTH AND SAFETY

2.1	An oc machir	An occurrence of catastrophic proportions, \checkmark resulting from the use of machinery, or activities at work. \checkmark	
2.2	The learner does not know safe practices. \checkmark The learner knows better but intentionally conducts the act.		(1)
2.3	2.3.1	Running could cause you to trip or collide with another learner. This could result in you injuring yourself with nearby equipment or machinery.	(2)
	2.3.2	This could cause the outlet to exceed its rated current \checkmark and could lead to short circuits, fires or damaged appliances. \checkmark	(2)
2.4	First, I would define all the various threats to safety in the workshop. \checkmark Secondly, I would determine the extent of all the vulnerabilities in the workshop. \checkmark		
	Finally	, I would devise countermeasures should a risk occur. \checkmark	(3) [10]

QUESTION 3: RLC CIRCUITS

(1) 3.1 3.1.1 It would remain the same. ✓

3.1.2
$$X_L = 31,83 \ \Omega \checkmark$$
 (1)

3.1.3 (a)
$$X_{L} = 2\pi f L \checkmark$$
$$= 2 \times \pi \times 50 \times 0.5 \checkmark$$
$$= 157,08 \Omega \checkmark$$
(3)

(b)
$$Z = \sqrt{R^2 + (X_L - X_C)^2} \checkmark$$

= $\sqrt{120^2 + (157,08 - 31,83)^2} \checkmark$
= 173,46 A \checkmark (3)

(c)
$$V_c = I \times X_c \checkmark$$

= 1,38 × 31,83 \checkmark
= 43,93 V \checkmark (3)

(d)
$$X_{C} = \frac{1}{2\pi fC}$$

 $C = \frac{1}{2\pi fX_{C}} \checkmark$
 $= \frac{1}{2 \times \pi \times 50 \times 42,44} \checkmark$
 $= 0,000075 F = 75 \mu F \checkmark$ (3)

(e)
$$I = \frac{V_R}{R} \checkmark$$
$$= \frac{240}{120} \checkmark$$
$$= 2 A \checkmark$$
 (3)

(1)

3.3 The small band of frequencies \checkmark centred around the resonant frequency. 🗸 The frequencies between the upper cut-off frequency and the lower cut-off (2) frequency, centred around the resonant frequency.

3.4 Z is maximum ✓ I is minimum ✓ $X_L = X_C$

3.5 3.5.1
$$I_{T} = \sqrt{I_{R}^{2} + (I_{C} - I_{L})^{2}} \checkmark$$
$$= \sqrt{0.83^{2} + (0.63 - 0.5)^{2}} \checkmark$$
$$= 0.84 \text{ A} \checkmark$$
(3)

3.5.2 I =
$$\frac{V}{R}$$

V = I. R \checkmark
= 0,83 × 120,487 \checkmark
= 100 V \checkmark (3)

(2)

$Z = \frac{V}{I_T} \checkmark$	
$=\frac{100}{0,84}$ \checkmark	
= 119,05 Ω ✓	(3)
	$Z = \frac{V}{I_{T}} \checkmark$ $= \frac{100}{0.84} \checkmark$ $= 119,05 \ \Omega \checkmark$

3.5.4
$$\cos\theta = \frac{I_R}{I_T}$$
$$\theta = \cos^{-1}\frac{I_R}{I_T} \checkmark$$
$$= \cos^{-1}\frac{0.83}{0.84} \checkmark$$
$$= 8,85^\circ \checkmark$$
leading \checkmark

(4) **[35]**

QUESTION 4: SEMICONDUCTOR DEVICES

4.1	Junction field effect transistor ✓	(1)
4.2	N-channel JFET or NFET 🗸	(2)

	P-Chanr	nel JFET or PFET 🗸	
4.3	To overo channel, means o	come leakage current between the gate terminal and drain-source the gate terminal was electrically isolated from the channel ✓ by f an extremely narrow layer of metal-oxide-silicon. ✓	(2)
4.4	4.4.1	Enhancement-mode 🗸 N-channel 🗸 MOSFET	(2)
	4.4.2	The lamp will switch ON as soon as the gate voltage V _{GS} is raised \checkmark to a sufficient level which will forward bias the internal channel of the MOSFET. \checkmark	(2)
	4.4.3	If R _{GS} is short circuited, it will cause the internal conductive channel of the MOSFET to disperse, \checkmark cutting the current flow \checkmark and switching the lamp OFF. \checkmark	(3)
4.5	4.5.1	 A – Cut off region ✓ D – Saturation region ✓ 	(2)
	4.5.2	At point C the UJT triggers ON. As the UJT is triggered, its internal resistance and voltage \checkmark will decrease \checkmark while current increases. \checkmark This is contrary to Ohm's law and is called negative resistance. At point D if the emitter is supplied with sufficient current the UJT operating point will continue falling until a valley point is reached (D), UJT goes into its permanent ON condition called saturation region.	(3)
4.6	4.6.1	Darlington pair ✓	(1)
	460	Very high current goin	

4.6.2 Very high current gain ✓
Improved input impedance ✓
When used in common collector pair it develops a very low output. (2)

(4)

(2)

(2)

(2)

- 4.7 Infinite gain ✓
 - Infinite input impedance ✓
 - Zero output impedance ✓
 - Infinite bandwidth ✓
 - Infinite common mode rejection ratio
 - Unconditional stability

4.8 4.8.1 $A_{V} = 1 + \frac{R_{F}}{R_{IN}} \checkmark$ $A_{V} = 1 + \frac{50\ 000}{10\ 000} \checkmark$ $A_{V} = 6 \checkmark$ (3) 4.8.2 $V_{OUT} = V_{IN} \times \left(1 + \frac{R_{F}}{R_{IN}}\right) V \checkmark$ $V_{OUT} = 1.5 \times \left(1 + \frac{50\ 000}{10\ 0000}\right) V \checkmark$

$$V_{OUT} = 9 V \checkmark$$
(3)
4.8.3 If the value of the feedback resistor is decreased the gain of the

- amplifier will decrease ✓ causing the output voltage to decrease. ✓ (2)
 4.9 4.9.1 This pin sets the voltage at which the 555 IC will trigger. It is used to maintain ✓ the voltage across the timing capacitor ✓ which is discharged through pin 7. ✓ (3)
 - 4.9.2 The 555 IC can operate from power supply voltages of between
 +5 V ✓ and +18 V. ✓
 - 4.9.3 In this mode the 555 timer is astable ('free running'), therefore its output will continuously toggle between high and low ✓ thus generating a continuous train of square-wave pulses. ✓
 - 4.9.4 The pin closest to the dot. ✓
 The pin to the left of the notch. (1)

4.10 Open loop gain is the gain of an op amp without any from the output to the input. ✓

Closed loop gain is the of an op amp with feedback from the output to the input. \checkmark

4.11 Basic timing functions like turning a light on or off ✓
 Pulse, oscillation and waveforms generation ✓
 Digital logic probes ✓
 Creating a warning light that flashes on and off
 Produce musical notes of a particular frequency
 (3)
 [45]
 [45]

QUESTION 5: SWITCHING CIRCUITS

5.1	5.1.1	Two external inputs ✓ Two stable states ✓	(2)
	5.1.2	The LED will be destroyed. ✓	(1)
	5.1.3	The current flowing through the LED will not be limited. \checkmark This will cause the LED to draw more current than what it is able to handle. \checkmark	(2)
	5.1.4	Pressing the SET button will pull Pin 2 "low" \checkmark and cause the IC output to switch to "high". \checkmark As Pin 6 is deliberately held "low" the IC cannot reset itself thus staying "high". \checkmark	(3)

5.1.5 These resistors are known as "pull up" resistors. ✓ When both SET and RESET buttons are open, the pull up resistors keep the voltage on the input high. ✓

(2)

7



- 5.3 The feedback resistor is connected from the output ✓ of the op amp to the inverting input. ✓ This allows a part of the output to flow back to the inverting input. ✓
- 5.4 It is used to eliminate switch bounce. ✓

(3) (1)

(6)

- The voltage divider feeds the non-inverting input of the op amp. ✓
- The inverting input is fed by a 100 k Ω variable resistor. \checkmark
- Less light on the LDR, the resistance rises and in turn the voltage on the non-inverting also rises. ✓
- When the voltage level increases to a level higher than the level set by the variable resistor, the op amp output will go high immediately. ✓
- This will switch the transistor on, and the alarm will be energized. ✓ (6)

5.6



5.7



5.8 5.8.1 A summing amplifier is used to add two or more different input signals \checkmark to create one amplified output signal. \checkmark (2)

5.8.2
$$V_{OUT} = -(V_1 + V_2 + V_3) \checkmark$$
$$= -(0,5+1,2+0,9) \checkmark$$
$$= -2.6 \lor \checkmark$$

OR

$$V_{OUT} = -\left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3}\right) V \checkmark$$

$$V_{OUT} = -\left(0.5 \frac{20\ 000}{20\ 000} + 1.2 \frac{20\ 000}{20\ 000} + 0.9 \frac{20\ 000}{20\ 000} V \checkmark$$

$$V_{OUT} = -2.6 V \checkmark$$
(3)

8

5.8.3
$$V_{OUT} = -\left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3}\right) V \checkmark$$
$$V_{OUT} = -\left(0.5 \frac{40\ 000}{5\ 000} + 1.2 \frac{40\ 000}{10\ 000} + 0.9 \frac{40\ 000}{20\ 000} V \checkmark$$
$$V_{OUT} = -10.6 V \checkmark$$
(3)

5.8.4
$$V_{OUT} = -\left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3}\right) V \checkmark$$
$$R_F = \frac{-V_{OUT}}{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}$$
$$R_F = \frac{-10.4}{\frac{0.5}{20\ 000} + \frac{1.2}{20\ 000} + \frac{0.9}{20\ 000}} \checkmark$$
$$R_F = 80\ k\Omega \checkmark$$

OR

$$A_V = -\frac{R_F}{R_{IN}}$$

$$R_F = A_V \times R_{IN}\Omega$$

$$R_F = 4 \times 20\ 000\ \Omega$$

$$R_F = 80\ 000\ \Omega$$

$$R_F = 80\ k\Omega$$

5.8.5

$$A_{V} = -\left(\frac{V_{OUT}}{V_{IN}}\right)$$
$$= -\left(\frac{V_{OUT}}{V_{1} + V_{2} + V_{3}}\right) \checkmark$$
$$= -\left(\frac{5,2}{0,5 + 1,2 + 0,9}\right) \checkmark$$
$$= -2 \checkmark$$

(3)

(3) **[50]**

Copyright reserved

QUESTION 6: AMPLIFIERS

6.1	Class / load lir	A – the transistor is biased with the Q-point on the midpoint \checkmark of the ne, allowing for the full signal (360°) to be amplified. \checkmark	(2)
6.2	6.2.1	C ₂ serves as the AC coupling component between the two stages. \checkmark C ₂ also blocks or decouples the DC component of the signal. \checkmark	(2)
	6.2.2	 When an AC voltage is applied to the input of the first amplifier stage, ✓an alternating current will flow in the collector circuit of transistor (Q1). ✓ An alternating voltage will develop across the collector resistor (Rc1). ✓ The developed alternating voltage across the Rc1 will be transferred through capacitor C2 ✓ to the base of the transistor (Q2) in the amplifier's second stage (stage 2). ✓ The process will be repeated and the amplified output will measured between C3 and 0 V. ✓ 	(6)
	6.2.3	 Impedance matching ✓ DC isolation ✓ Correct frequency response (Any 2 x 1) 	(2)
6.3	6.3.1	 A – Low frequencies ✓ B – Middle frequencies ✓ C – High frequencies ✓ D – Voltage gain ✓ 	(4)
	6.3.2	Frequency response is the ability of the circuit \checkmark to respond to a range of frequencies applied to the transistor. \checkmark	(2)
	6.3.3	At lower frequencies the reactances of the decoupling capacitors across the emitter resistors rises. \checkmark These reactances each combine with the resistance of their emitter resistors, causing the total impedance to rise \checkmark limiting the stage gain. \checkmark	(3)
6.4	6.4.1	Impedance matching can be achieved by selecting a transformer \checkmark with the required number of turns \checkmark that will coincide with the impedances of the respective stages.	(2)
	6.4.2	The reason for using a transformer is that the relatively high output impedance of the second stage \checkmark is connected to the relatively low impedance of the speaker \checkmark thus matching the output impedance \checkmark of the amplifier to the load.	(3)

	6.4.3	Poor frequency response – gain is constant over only a small range of frequencies ✓ Coupling transformers are bulky and expensive at audio frequencies ✓ Low frequencies receive less amplification than high frequencies Tends to introduce hum in the output Increased cost	(2)
6.5	6.5.1	An oscillator is a device which generates an AC output signal \checkmark without any externally applied input signal. \checkmark	(2)
	6.5.2	The RF coil resistance against the change in the collector current \checkmark and causes the collector voltage Vc to decrease. \checkmark	(2)
	6.5.3	The resistors R ₁ and R ₂ form a voltage divider \checkmark to bias the base of the transistor. \checkmark	(2)
	6.5.4	The Colpitts oscillator uses TWO capacitors and an inductor in the tank circuit. \checkmark The Hartley oscillator uses TWO inductors and a capacitor in the tank circuit. \checkmark	(2)
	6.5.5	When first switched ON, the collector voltage rises and allows the capacitor in the tank circuit to charge. \checkmark The voltage drop across the inductors is in an inverted form, driving the transistor's base in the opposite direction thereby switching it OFF. \checkmark The capacitor will discharge through the inductors and push the tank circuit into oscillation. \checkmark During oscillation the voltages at each end of the tank circuit are 180° out of phase with each other, relative to their 0 V common centre tap point. \checkmark This ensures that the collector voltage is 180° out of phase with the base voltage. \checkmark The freewheeling effect of the tank circuit's operation then begins to drive the transistor alternately ON and OFF which in turn continually re-charges the tank circuit keeping it oscillating at a constant \checkmark amplitude.	(6)
	6.5.6	$F_{O} = \frac{1}{2\pi\sqrt{L \times C}} \checkmark$	(0)
		$L_T = L_1 + L_2 \checkmark$	(2) [45]

TOTAL: 200